1

Assignment No.1

Dukkipati Vijay Sai

Download all python codes from

https://github.com/dukkipativijay/Fwciith2022/blob/main/Assignment1.cpp

and latex-tikz codes from

https://github.com/dukkipativijay/Fwciith2022/blob/main/Assignment%201/Latex%20File.tex

1 Question-2016 Section C Q6(d)

Reduce the following Boolean Expression to its simplest form using k-map $F = (X, Y, Z, W) = \sum (2, 6, 7, 8, 9, 10, 11, 13, 14, 15)$

2 Contents

Components3Hardware4Solution5

Abstract- This manual shows how to use 7447 BCD-seven segment display encoder to display Boolean Logic

3 Components

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

Table 3.0

4 Hardware

Make connections between seven segment display and the 7447 ic as per the given table

7447	a'	b'	c'	ď'	e'	f'	g'
Display	a	b	c	d	e	f	g

Table 4.0

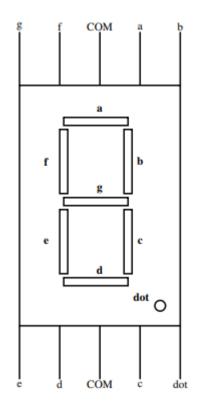


Figure 1

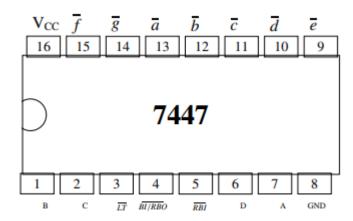


Figure 2

7447	D	С	В	A
Arduino	5	4	3	2

Table 4.1						
	X	Y	Z	W		
Input	0	1	1	0		
Arduino	6	7	8	9		

Table 4.2

In the above example we are taking number 6 as input to the arduino and displaying 1 on the seven segment display.

5 Solution

Truth Table							
X	Y	Z	W	F			
0	0	0	0	0			
0	0	0	1	0			
0	0	1	0	1			
0	0	1	1	0			
0	1	0	0	0			
0	1	0	1	0			
0	1	1	0	1			
0	1	1	1	1			
1	0	0	0	1			
1	0	0	1	1			
1	0	1	0	1			
1	0	1	1	1			
1	1	0	0	0			
1	1	0	1	1			
1	1	1	0	1			
1	1	1	1	1			

Table 5.0

$\setminus ZW$						
XY	00	01	11	10		
00	0	0	0	1		
01	0	0	1	1		
11	0	1	1	1		
10	1	1	1	1		

Table 5.1

The expression in the above k-map results in XY'

XY	W 00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.2

The expression in the above map k-map results in XW

XY	W 00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.3

The expression in the above map k-map results in XZ

XY	W 00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.4

The expression in the above k-map results in YZ

$\setminus Z$				
XY	00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.5

The expression in the above k-map results in ZW' By solving the above Karnaugh Map, we get the simplified boolean expression given below

$$F = XY' + XW + XZ + YZ + ZW'$$