

# Assignment No.1

Dukkipati Vijay Sai

Download IDE code from

<https://github.com/dukkipativijay/Fwciith2022/blob/main/Assignment1.cpp>

Download Assembly code from

<https://github.com/dukkipativijay/Fwciith2022/tree/main/Assignment%201/Codes/asm>

Download GCC code from

<https://github.com/dukkipativijay/Fwciith2022/blob/main/Assignment%201%20-%20GCC/main.c>

and latex-tikz codes from

<https://github.com/dukkipativijay/Fwciith2022/blob/main/Assignment%201/Latex%20File.tex>

## 1 QUESTION-2016 SECTION C Q6(D)

Reduce the following Boolean Expression to its simplest form using k-map  $F = (X, Y, Z, W) = \sum(2, 6, 7, 8, 9, 10, 11, 13, 14, 15)$

## 2 CONTENTS

Components	3
Hardware	4
Solution	5

*Abstract-* This manual shows how to use 7447 BCD-seven segment display encoder to display Boolean Logic

## 3 COMPONENTS

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

Table 3.0

## 4 HARDWARE

Make connections between seven segment display and the 7447 ic as per the given table

7447	a'	b'	c'	d'	e'	f'	g'
Display	a	b	c	d	e	f	g

Table 4.0


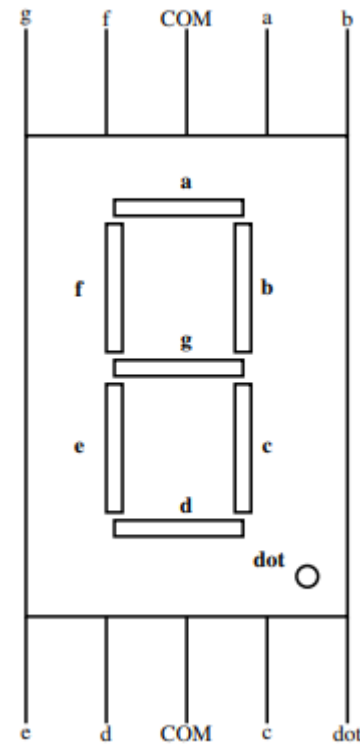


Figure 1

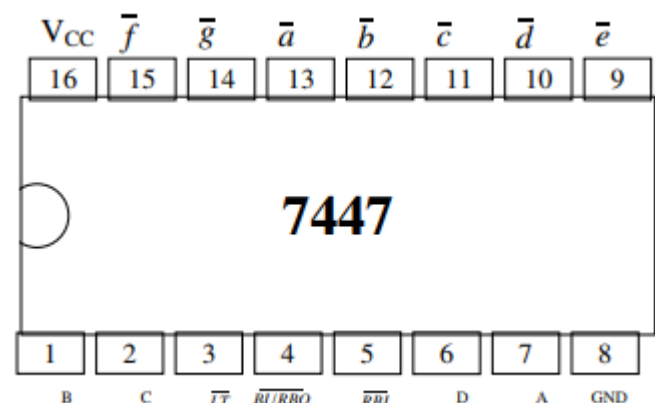

**Figure 2**

<b>7447</b>	D	C	B	A
<b>Arduino</b>	5	4	3	2

Table 4.1

	X	Y	Z	W
<b>Input</b>	0	1	1	0
<b>Arduino</b>	6	7	8	9

Table 4.2

In the above example we are taking number 6 as input to the arduino and displaying 1 on the seven segment display.

## 5 SOLUTION

**Truth Table**

X	Y	Z	W	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Table 5.0

XY \ ZW	00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.1

The expression in the above k-map results in  $XY'$

XY \ ZW	00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.2

The expression in the above map k-map results in  $XW$

XY \ ZW	00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.3

The expression in the above map k-map results in  $XZ$

XY \ ZW	00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.4

The expression in the above k-map results in  $YZ$

XY \ ZW	00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	0	1	1	1
10	1	1	1	1

Table 5.5

The expression in the above k-map results in  $ZW'$

By solving the above Karnaugh Map, we get the simplified boolean expression given below

$$F = XY' + XW + XZ + YZ + ZW'$$